

# **EE-227: Digital Logic & Design**

Serial No:

**Final Exam**

**Total Time: 3 Hours**

**Total Marks: 100**

Tuesday, 24<sup>th</sup> December, 2019

**Course Instructors**

SHAMS FAROOQ

\_\_\_\_\_  
Signature of Invigilator

\_\_\_\_\_  
Student Name

\_\_\_\_\_  
Roll No

\_\_\_\_\_  
Section

\_\_\_\_\_  
Signature

**DO NOT OPEN THE QUESTION BOOK OR START UNTIL INSTRUCTED.**


**Instructions:**

1. Attempt on question paper. Attempt all of them. Read the question carefully, understand the question, and then attempt it.
2. No additional sheet will be provided for rough work. Use the back of the last page for rough work.
3. If you need more space write on the back side of the paper and clearly mark question and part number etc.
4. After asked to commence the exam, please verify that you have twenty (20) different printed pages including this title page. There are a total of 8 questions.
5. Calculator sharing is strictly prohibited.
6. Use permanent ink pens only. Any part done using soft pencil will not be marked and cannot be claimed for rechecking.

	Q-1	Q-2	Q-3	Q-4	Q-5	Q-6	Q-7	Q-8	Total
Marks Obtained									
Total Marks	10	10	10	15	15	15	10	15	100

## **Question 1 [5+5 Marks]**

 
a. Design **2x4 Decoder** using following block diagram?



### **TRUTH TABLE**


### **EXPRESSIONS**

 **b. Design 2x4 High Priority Encoder? Where Y3 has more priority over Y2**




## **TRUTH TABLE**


## **EXPRESSIONS**



b. Use block diagram given above to create **8x1 Multiplexer**?

 c. For the multiplexer given below, determine output **Y** (Timing Diagram) with **data select inputs  $S_0$  and  $S_1$**  to the multiplexer are sequenced as shown in waveform given below, where  **$D_0=0, D_1=1, D_2=1, D_3=0$** .



**Y**

**Question 3 [5+5 Marks]**

*a. Design Invalid BCD Detector circuit?*

**TRUTH TABLE**

---

---

---

---

---

---

---

---





---

---

**SIMPLIFICATION**

    **EXPRESSION**





- b.** Modify Circuit given below by adding INVALID DETECTOR Circuit designed above so circuit is able to add BCD number  $(96)_{bcd} + (85)_{BCD}$







**Question 4 [6 +6+ 3 Marks]**

a. Process each state given below to find values of  $Q_{t+1}$  and  $\bar{Q}_{t+1}$ ? Fill the results in a table?

**CASE I**





 
 
 
 


**CASE II**

    




        b. Process the following circuit and produce table.



$CLK$	$J$	$K$	$Q_{t+1}$	$\overline{Q}_{t+1}$

 c. Modify given circuit to introduce Asynchronous **CLEAR** and **SET** inputs fill table




SET	CLEAR	$Q_{t+1}$	$\overline{Q}_{t+1}$
0	0		
0	1		
1	0		
1	1		



 d. Following is a **74LS93** is a 4-bit Asynchronous Counter logic diagram? Convert it to **Decade Counter**?

**NOTE:** You are not supposed to use any additional gates



## Question 6 [4+3+4+4= 15 Marks]

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
<i>a</i>	<i>f</i>	<i>b</i>	0	0
<i>b</i>	<i>d</i>	<i>c</i>	0	0
<i>c</i>	<i>f</i>	<i>e</i>	0	0
<i>d</i>	<i>g</i>	<i>a</i>	1	0
<i>e</i>	<i>d</i>	<i>c</i>	0	0
<i>f</i>	<i>f</i>	<i>b</i>	1	1
<i>g</i>	<i>g</i>	<i>h</i>	0	1
<i>h</i>	<i>g</i>	<i>a</i>	1	0

a. *For the Following state table. Draw the corresponding state diagram*



b. *Tabulate the reduce table*

c. Draw the state diagram corresponding to the reduce state table



d. Starting from A and the input sequence **01110010011**, Determine output sequence for actual and reduce state diagram

## Question 7 [5+5]

 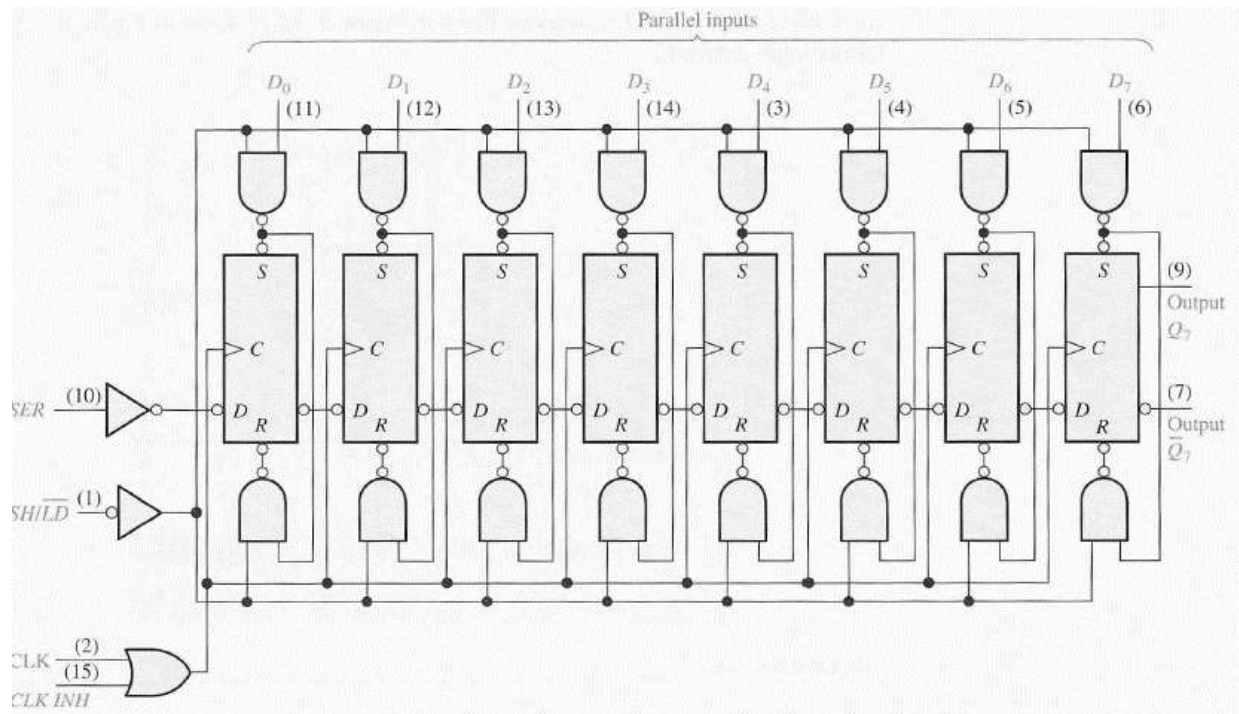a. Name the following circuit? Complete Timing Diagram fill  $Q_7$ .



 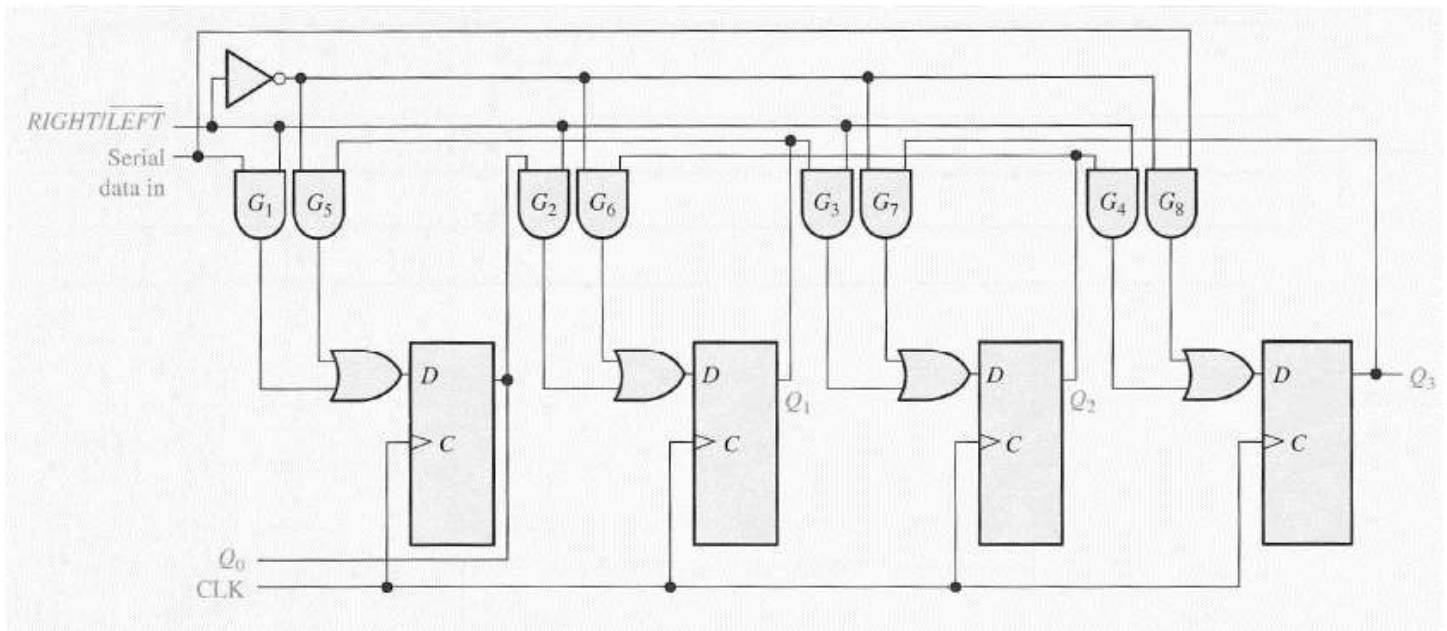- b. Name the following circuit? Complete Timing Diagram assume  $Q_0=1$ ,  $Q_1=1$ ,  $Q_2=0$  and  $Q_3=1$  and that **serial Data input** line is **LOW**





**Question 8 [15 Marks]**

Design **UP/DOWN Counter** using **JK Flip-Flop** to produce following sequence **1,4,3,5,7,6,2...** when  $x=0$  counter Counts and for  $x=1$  counter count down? Draw State diagram, State Transition table, K-map, Extract expression where least significant flip-flop is named A with  $J_A$  and  $K_A$  inputs Output is  $Q_A$



**ROUGH PAGE**

**ROUGH PAGE**